



IMPLEMENTATION OF KMAP BOOLEAN LOGIC WITH ARDUINO

Ch.Pranai

pranai.fwc1@iiitb.ac.in

COMETFWC022

IITB Future Wireless Communication (FWC)

ASSIGNMENT

July 06, 2025

Abstract

The minimal sum-of-products expression for the logic function f represented by the given Karnaugh map is:

PQ/RS	00	01	11	10
00	0	1	0	0
01	0	1	1	1
11	1	1	1	0
10	0	0	1	0

Options:

- (A) $QS + \overline{P}\overline{R}S + \overline{P}QR + PRS + \overline{P}QR$ —
- (B) $QS + \overline{P}\overline{R}S + \overline{P}QR + PRS$ —
- (C) $\overline{P}\overline{R}S + PQR + PRS + \overline{P}QR$ —
- (D) $\overline{P}\overline{R}S + PQR + PQR$ —

Kmap

PQ/RS	00	01	11	10
00	0	1	0	0
01	0	1	1	1
11	1	1	1	0
10	0	0	1	0

Components

Component	Value	Quantity
ArduinoBoard	– M-F – – – –	1
JumperWires	220 Ω , 10k Ω	1
PushButtons		0
Breadboard		4
USBCable		1
LED		1
Resistors		1

5

Setup

1. Connect buttons to pins D2–D5 for inputs P, Q, R, S, each with a 10k Ω pull-down resistor to ground.
2. Connect an LED to pin D13 through a 220 Ω resistor to ground.
3. Write Arduino code to read inputs and compute $f = !P \cdot R \cdot S + P \cdot Q \cdot R + !P \cdot R \cdot !S + !P \cdot Q \cdot R$.
4. Use `digitalWrite(13, f)` to control the LED based on the computed output.
5. Upload the code and test by pressing buttons to check when the LED turns ON for $f = 1$.

Implementation

Connect push buttons to pins D2–D5 for inputs P, Q, R, S with 10k Ω pull-down resistors.

Connect an LED to pin D13 through a 220 Ω resistor to ground.

Write Arduino code to read inputs and compute $f = !P \cdot R \cdot S + P \cdot Q \cdot R + !P \cdot R \cdot !S + !P \cdot Q \cdot R$.

Use `digitalWrite(13, f)` to control the LED based on the computed output.

Upload the code and test by pressing buttons to check when the LED turns ON for $f = 1$.