



# IMPLEMENTATION OF 2-INPUT AND XOR LOGIC ON ARDUINO

Ch.Pranai

pranai.fwc1@iitb.ac.in

COMETFWC022

IITB Future Wireless Communication (FWC)

ASSIGNMENT

July 06, 2025

## Question

What are the minimum number of 2-to-1 multiplexers required to generate a 2-input AND gate and a 2-input Ex-OR gate?

- (A) 1 and 2
- (B) 1 and 3
- (C) 1 and 1
- (D) 2 and 2

## Components

Component	Value	Quantity
Arduino Board	–	1
Jumper Wires	M-F	10
Push Buttons	–	2
Breadboard	–	1
USB Cable	–	1
LED (Optional)	–	2
7-Segment Display Common Cathode		
Resistors	220Ω, 10kΩ	

## Truth Table for 2-input AND and XOR using MUX

A	B	AND(A·B)	XOR (A ⊕ B)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

## Setup

1. Connect two push buttons to digital pins D2 and D3 with 10kΩ pull-down resistors as inputs A and B.

2. Connect a common cathode 7-segment display to Arduino digital pins D4–D10 for segments a–g.

3. Write code to read button states using digitalRead(D2) and digitalRead(D3).

4. Use logic to calculate A AND B and A XOR B and store results.

5. Display AND output on one digit and XOR output on another using segment encoding.

# Implementation

1. Define input pins for push buttons A and B and output pins for 7-segment display segments.
2. Initialize all pin modes in setup() using pinMode() for inputs and outputs.
3. Read button values using digitalRead() and store them in variables a and b.
4. Compute  $\text{andresult} = a \& b$  and  $\text{xor result} = a \wedge b$ .
5. Use digitalWrite() to display andresult and xorresult on respective 7-segment digits.