



# IMPLEMENTATION OF LOGIC EXPRESSION WITH ARDUINO

Ch Pranai

pranai.fwc1@iiitb.ac.in

COMETFWC022

IITB Future Wireless Communication (FWC)

ASSIGNMENT

July 06, 2025

## Abstract

Q.36  $X = 1$  in the logic equation  

$$[x + \frac{(If}{Z} \frac{Y}{Y} + (\bar{Z} + XY) ) ] (\bar{X} + Z(\bar{X} + Y)) = 1,$$

then:

- (A)  $Y = Z$
- (B)  $Y = \bar{Z}$
- (C)  $Z = 1$
- (D)  $Z = 0$

## Components

Component	Value	Quantity
Arduino Board	– M-F – – – –	1 10 2 1 1
Jumper Wires	220Ω, 10kΩ	1 1, 2
Push Buttons		
Breadboard		
USB Cable		
LED		
Resistors		

## Truth Table for $f = \bar{Z}(1 + Y)$

	Z	$\bar{Z}$	$1 + Y$	$f = \bar{Z}(1 + Y)$
	0	1	0 1	1 0 1
	1	0	1 1	0
	0	1	1 1	
	1	0	1	

## Setup

1. Connect push button for Y to D2 with a 10kΩ pull-down resistor to GND.
2. Connect push button for Z to D3 with a 10kΩ pull-down resistor to GND.
3. Connect LED anode to D13 through a 220Ω resistor, and cathode to GND.
4. Upload the Arduino code that reads Y and Z, sets  $X = 1$ , evaluates logic, and controls the LED.
5. Power the Arduino using a USB cable or external 5V source to run the circuit.

# Implementation

1. Set  $X = 1$  directly in the Arduino code.
2. Read  $Y$  from digital pin D2 and  $Z$  from D3 using `digitalRead()`.
3. Compute  $\text{not}Z = !Z$  to evaluate the simplified logic expression.
4. Use the result ( $\text{not}Z$ ) to control the LED with `digitalWrite(13, result)`.
5. Continuously run the logic in the `loop()` function to respond to input changes.